

# CPE166 Advanced Logic Design

Introduction

Professor Jing Pang


# Advantage of Digital Devices

- Reproducibility of information
- Flexibility and functionality: easier to store, transmit and manipulate information
- Economy: cheaper device and easier to design
- Moore's law
  - Transistor geometry
  - Chips double its density (number of transistor) in every 18 months
  - Devices become smaller, faster and cheaper

# Two HDLs (Hardware Description Languages) Used Today

- VHDL and Verilog
- Syntax and "appearance" of the two languages are very different
- Both are IEEE and industrial standards

# Components of a Verilog Module

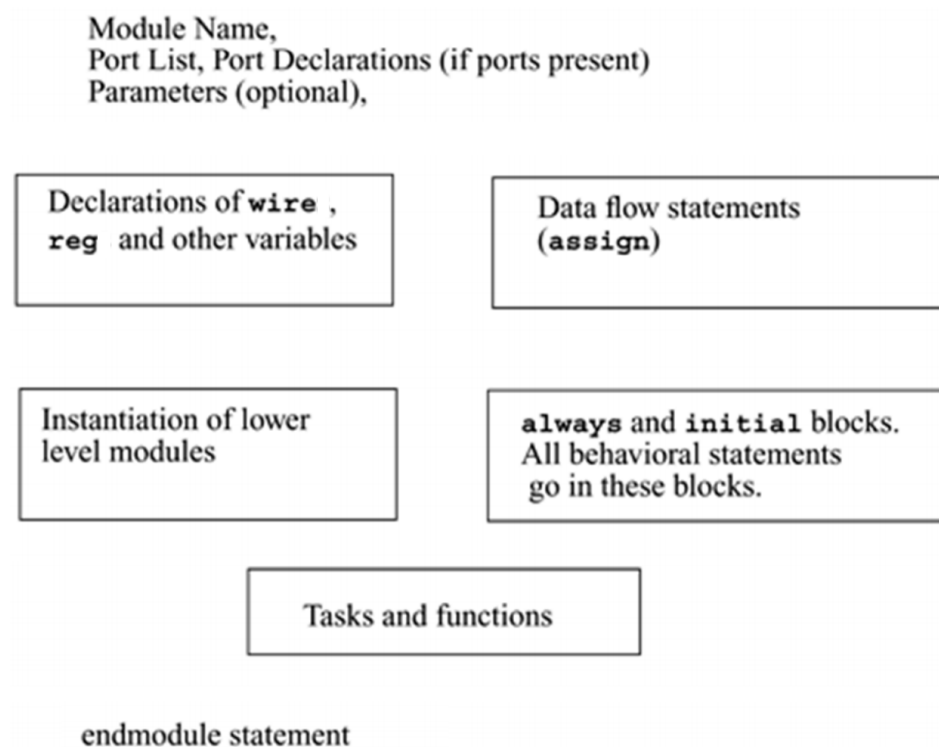

# Nesting of Modules

In Verilog nesting of modules is not permitted i.e., one module definition cannot contain another module definition within the module and endmodule statements.



**Example:**

```
module counter(q, clk, reset);  
output [3:0]q;  
input clk, reset;  
  
    module T_FF(q, clock, reset) // Illegal  
    .  
        endmodule  
endmodule
```

# Structural Design

```
module half_adder (a,b,s,c);  
output s,c;  
input a, b;  
wire s, c;  
xor g1 (s,a,b);  
and g2(c,a,b);  
endmodule
```

Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

  

```

module ha(a,b,s,c);
output s,c;
input a, b;
wire s, c;
xor g1(s,a,b);
and g2(c,a,b);
endmodule


```

```

module ha_tb;
reg a, b;
wire s, c;
ha hh(a,b,s,c);
initial
begin
    a=0; b=0;
end
always
begin
    #2 a=1; b=0;
    #2 a=0; b=1;
    #2 a=1; b=1;
    #2 a=0; b=0;
end
initial $monitor($time, ". a=%b, b=%b, carry=%b, sum=%b", a, b, c, s);
initial #24 $stop;
endmodule

```

0.	a=0,	b=0,	carry=0,	sum=0
2.	a=1,	b=0,	carry=0,	sum=1
4.	a=0,	b=1,	carry=0,	sum=1
6.	a=1,	b=1,	carry=1,	sum=0
8.	a=0,	b=0,	carry=0,	sum=0
10.	a=1,	b=0,	carry=0,	sum=1
12.	a=0,	b=1,	carry=0,	sum=1
14.	a=1,	b=1,	carry=1,	sum=0
16.	a=0,	b=0,	carry=0,	sum=0
18.	a=1,	b=0,	carry=0,	sum=1
20.	a=0,	b=1,	carry=0,	sum=1
22.	a=1,	b=1,	carry=1,	sum=0

 


# 2-to-4 Decoder

```
module dec2_4(a, b, en);
output [3:0] a;
input [1:0] b;
input en;
wire [1:0] bb;
```

```
not g1(bb[1], b[1]), (bb[0], b[0]);
and g2 (a[0], en, bb[1], bb[0]);
and g3 (a[1], en, bb[1], b[0]);
and g4 (a[2], en, b[1], bb[0]);
and g5 (a[3], en, b[1], b[0]);
endmodule
```

```
module dec2_4_tb;
wire [3:0] a;
reg [1:0] b;
reg en;
dec2_4 uut(a, b, en);
initial
begin
    { b, en } = 3'b000;
    #2 { b, en } = 3'b001;
    #2 { b, en } = 3'b011;
    #2 { b, en } = 3'b101;
    #2 { b, en } = 3'b111;
end
initial
    $monitor ($time, " output a=%b, input b=%b, input en=%b", a, b, en);
endmodule
```

0	output a=0000,	input b=00,	input en=0
2	output a=0001,	input b=00,	input en=1
4	output a=0010,	input b=01,	input en=1
6	output a=0100,	input b=10,	input en=1
8	output a=1000,	input b=11,	input en=1

 



# Data Flow Design

```
module half_adder (a,b,s,c);  
output s,c;  
input a,b;  
wire s,c;  
assign s=a ^b;  
assign c= a & b;  
endmodule
```


# Behavioral Design

```
module ex (a,b,s,c);  
output s,c;  
input a,b;  
reg s,c;  
always @(a or b)  
begin  
    if (a==0 && b==0)  
        begin  
            s=1'b0; c=1'b0;  
        end  
end
```

```
else if ((a==1 && b==0) || (a==0 && b==1))  
    begin  
        s=1'b1; c=1'b0;  
    end  
else  
    begin  
        s=1'b0; c=1'b1;  
    end  
end  
  
endmodule
```
 
# Concurrency

In an electronic circuit all the units are to be active and functioning concurrently.



If (*a*, *b*, *c* or *d* changes)

**update** *e* as

$$e = \overline{a.b + c.d}$$

```
module test_and;
reg a1, a2;
wire b;
initial
begin
    a1=0; a2=0;
    #3 a1=1;
    #3 a1=0;
    a2=1;
    #3 a1 =1;
    #10 $stop;
end
and g1(b, a1, a2);
initial $monitor($time, "a1=%b, a2=%b, b=%b", a1, a2, b);
initial #100 $finish;
endmodule
```

0	a1=0,	a2=0,	b=0
3	a1=1,	a2=0,	b=0
6	a1=0,	a2=1,	b=0
9	a1=1,	a2=1,	b=1

# Verilog Constructs and Conventions

- Operators

- unary operators: operates on a single operand.

- assign out = ~ a;

- binary operators: operates on two operands.

- assign out = a & b;

- ternary operators: operates on three operands.

- assign out = s ? a : b;

# Comments

– single / one line comment example:

```
module d_ff (Q, dp, clk);  
//This is the design description of a D flip-flop.
```

– multiple line / block comment Example:

```
/* this logic performs  
   even parity design of  
   multiple binary bits */
```

# Identifiers

- Identifiers are used to define language constructs.
- Identifiers refer objects to be referenced in the design.
- Identifiers are made of alphabets (both cases), numbers, the underscore ‘\_’ and the dollar sign ‘\$’.
- They start with an alphabetic character or underscore.
- They cannot start with a number or with ‘\$’ which is reserved for system tasks.
- Identifiers are case sensitive i.e., identifiers differing in their case are distinct.
- An identifier say count is different from COUNT, count and cOuNT.

# Identifiers

- **name, \_name. Name, name1, name\_\$, . . .** all these are allowed as identifiers
- **name aa** not allowed as an identifier because of the blank ( “name” and “aa” are interpreted as two different identifiers)
- **\$name** not allowed as an identifier because of the presence of “\$” as the first character.
- **1\_name** not allowed as an identifier, since the numeral “1” is the first character
- **@name** not allowed as an identifier because of the presence of the character “@”.
- **A+b** not allowed as an identifier because of the presence of the character “+”.



# String

A string is a sequence of characters enclosed within double quotes.

A string must be contained on a single line.

Special characters are specified by preceding them with the  
"\" character.

```
"This is a string"
```

```
"This string is one \t with a gap in between"
```

```
"This is called a \"string\""
```

# Examples for Identifiers

Count

COUNT

\_R2\_D2

R56\_68


FIVE\$

\$count

Illegal

12six\_b

Illegal

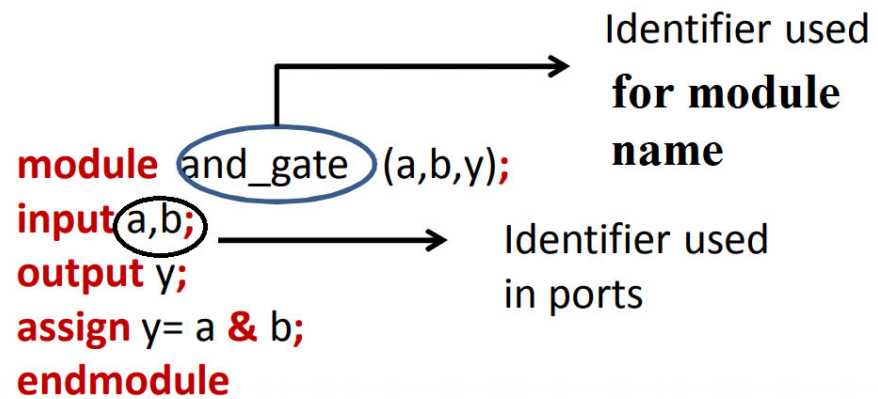

# Keywords

Verilog HDL is case-sensitive.

All the keywords in Verilog must be in lower case.

**module** → signifies the beginning of a module definition.

**endmodule** → signifies the end of a module definition.

**begin** → signifies the beginning of a block of statements.

**end** → signifies the end of a block of statements.

**if** → signifies a conditional activity to be checked

# Number Specification

Sized numbers.

<size> '<base format> <number>

'Unsize numbers.

'<base format> <number>

<size> in decimal

<base format> can be b or B, d or D, o or O and h or H.

Numbers without <base format> are decimal by default.

# Logic Values

1: logic high

0: logic low

x: unknown or uninitialized

z: high impedance or left floating

# Numbers

- Sized numbers :

4'b1111 // This is a 4-bit binary number

12'habc // This is a 12-bit hexadecimal number

16'd255 // This is a 16-bit decimal number.

32 'B z // this is a 32-bit high impedance number

6 'h x // this is a 6-bit hex number

- Unsized numbers :

23456 // This is a 32-bit decimal number by default

'hc3 // This is a 32-bit hexadecimal number

'o21 // This is a 32-bit octal number

# Numbers

5'037	5-bit octal
4'D2	4-bit decimal
9'b11011x01	x signifies the concerned bit to be of unknown value.
9'o12z	equivalent to 001 010 <b>zzz</b>
7'Hx	7-bit x (x extended), i.e.... xxxxxxx
4'hz	4-bit z (z extended), i.e... zzzz
4'd-4	Not legal
-4'd7	Its value in 2's complement form is 7.
8 'h 2A	Spaces allowed between size & ' character & between <i>base</i> and <i>value</i>
3' b001	Not legal: no space allowed between ' and base b
10'b10	Padded with 0 to the left, 0000000010
11'hb0	equivalent value is 000 1011 0000.
5'hza	A 5-bit hex number. Its value is taken as <b>z</b> 1010.
3'b1001_0011	is same as 3'b011

# Scalars, Vectors & Parameters

```
wire m;           // scalar wire type data m
reg n;           // scalar reg type data n
wire [3:0] a;     /* a is a 4-bit vector of wire type; the bits are designated as
                  a[3], a[2], a[1], and a[0] */

reg [2:0] b;     /* b is a 3-bit vector of reg type; the bits are designated as
                  b[2], b[1], and b[0] */

wire signed [4:0] num; // num is a vector in the range -16 to +15
reg signed [3:0] num2; // num2 is a vector in the range -8 to 7

parameter m = 3, n=5;
```



# Strings & White Space

## Strings

- A string is a sequence of characters enclosed by double quotes.
- Spaces are not ignored in strings.
- Strings cannot be on multiple lines.

## White Space

- Blank spaces ---> `\b`
- Tabs ---> `\t`
- New lines ---> `\n`
- White space is not ignored in strings.
- Example:  $\$display($  “The value of  $a=%b$ ,  $b=%b$ ,  $y=%b \n$ ”,  $a,b,y$ );